

Review on Digital Design (Sequential Circuits)

University of South Carolina

Introduction to Computer Architecture

Fall, 2024

Mehdi Yaghouti



**Molinaroli College of
Engineering and Computing**

UNIVERSITY OF SOUTH CAROLINA

Storage Elements


- Maintains a binary state as long as power is on
- Provides control signals to switch the state
- Level sensitive storage elements: Latches
- Transition sensitive storage elements: Flip-Flops
- Latches are the building blocks of Flip-Flops
- Latches are useful for asynchronous designs
- Flip-Flops are the choice for synchronous circuits

Latches

- Latches are level sensitive
- S and R stand for Set and Reset
- $S = 1, R = 0$ set the output
- $S = 0, R = 1$ reset the output
- $S = 0, R = 0$ retains the old value
- $S = 1, R = 1$ causes race condition (forbidden)




S	R	Q	Q'
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$)
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$)
1	1	0	0 (forbidden)

 


D-Latches

 - Latches are level sensitive
- S and R stand for Set and Reset
- $S = 1, R = 0$ set the output
- $S = 0, R = 1$ reset the output
- $S = 0, R = 0$ retains the old value
- $S = 1, R = 1$ causes race condition (forbidden)
- D-Latch eliminates the forbidden status



S	R	Q	Q'
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$)
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$)
1	1	0	0 (forbidden)

 

D-Latches

- Latches are level sensitive
- S and R stand for Set and Reset
- $S = 1, R = 0$ set the output
- $S = 0, R = 1$ reset the output
- $S = 0, R = 0$ retains the old value
- $S = 1, R = 1$ causes race condition (forbidden)
- D-Latch eliminates the forbidden status
- Clk determines when change is allowed




S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0


(after $S = 1, R = 0$)

(after $S = 0, R = 1$)

(forbidden)



 


Clk	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

 






D Flip-Flop

   - Master and Slave D-Latches connected back to back
- Master and Slave receives complementary clocks
- At $Clk = 1$, Master Latch is transparent
- At $Clk = 0$, Slave Latch is transparent





Register

     - Enable determines whether data is loaded
- Reset clear the output to 0
- N-bit register is a bank of N Flip-Flops




Register File

  - 4×4-bits register file
- 2 Read ports
- 1 Write port
- $\log_2 4$ address bus
- 32×32-bits register file



Synchronous Sequential Circuits

 - The outputs and the next state are both a function of the inputs
- The state of the system is hold in flip flops




Finite State Machines

- Synchronous sequential circuits can be designed as Finite State Machines
- At each clock both the state and the output of the circuit will be updated
- The next state is computed based on both input and the current state


Finite State Machines

 - Synchronous sequential circuits can be designed as Finite State Machines
- At each clock both the state and the output of the circuit will be updated
- The next state is computed based on both input and the current state
- There are two type of FSM
 - **Moore machines:** The output depends directly only on the current state




Finite State Machines

 - Synchronous sequential circuits can be designed as Finite State Machines
- At each clock both the state and the output of the circuit will be updated
- The next state is computed based on both input and the current state
- There are two type of FSM
 - **Moore machines:** The output depends directly only on the current state



 - **Mealy machines:** The output depends on both current state and the input



State Diagram

- **State Diagram:**

A visual representation that depicts state transitions and outcomes in response to inputs


- **States:** Different conditions a system can be in
- **Transitions:** Arrows showing movement between states
- **Inputs:** Triggers for state changes
- **Reset state:** Start and end points of the process
- **State Actions:** Actions within states or during transitions

State Diagram

- **State Diagram:**

A visual representation that depicts state transitions and outcomes in response to inputs

 - **States:** Different conditions a system can be in
- **Transitions:** Arrows showing movement between states
- **Inputs:** Triggers for state changes
- **Reset state:** Start and end points of the process
- **State Actions:** Actions within states or during transitions





State Diagram

- **State Diagram:**

A visual representation that depicts state transitions and outcomes in response to inputs

  - **States:** Different conditions a system can be in
- **Transitions:** Arrows showing movement between states
- **Inputs:** Triggers for state changes
- **Reset state:** Start and end points of the process
- **State Actions:** Actions within states or during transitions



Moore Machine Design


④ Assigning binary codes to states

$S_0 \rightarrow 00$

$S_1 \rightarrow 01$

$S_2 \rightarrow 10$

$S_3 \rightarrow 11$

 


- State coding is not unique and will affect the design

Moore Machine Design

- 1 Assigning binary codes to states
- 2 Obtain the binary-coded state table

Present State		Input	Next State	
S_1	S_0		S'_1	S'_0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1

 

Moore Machine Design

- 1 Assigning binary codes to states
- 2 Obtain the binary-coded state table
- 3 Obtain the equations for flip flops inputs

Present State		Input	Next State	
S_1	S_0	x	S'_1	S'_0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1

$$S'_0 = S_1 S_0 x + S_1 \overline{S_0} \overline{x} + \overline{S_1} \overline{S_0} x$$

$$S'_1 = S_1 \overline{S_0} + \overline{S_1} S_0 x$$

Moore Machine Design


- 1 Assigning binary codes to states
- 2 Obtain the binary-coded state table
- 3 Obtain the equations for flip flops inputs
- 4 Obtain the output equations in terms of states

Present State		Output
S_1	S_0	y
0	0	0
0	0	0
0	1	0
0	1	0
1	0	0
1	0	0
1	1	1
1	1	1

$$y = S_1 S_0$$

Moore Machine Design

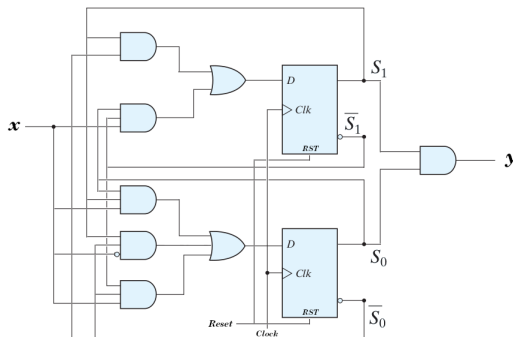- 1 Assigning binary codes to states
- 2 Obtain the binary-coded state table
- 3 Obtain the equations for flip flops inputs
- 4 Obtain the output equations in terms of states
- 5 Draw the logic circuit diagram



SystemVerilog

- Moore's FSM implementation
- typedef, always_ff, always_comb



```
module moore_FSM ( input logic clk,  
                  input logic reset,  
                  input logic a,  
                  output logic y );
```

```
    typedef enum logic [1:0] {S0,S1,S2,S3} State;  
    State curr_state, next_state;
```

```
    always_ff @(posedge clk, posedge reset)  
        if (reset) curr_state <= S0  
        else curr_state <= next_state;
```

```
    always_comb  
        case (curr_state)  
            S0: if (a) next_state = S1;  
                else next_state = S0;  
            S1: if (a) next_state = S2;  
                else next_state = S0;  
            S2: if (a) next_state = S2;  
                else next_state = S3;  
            S3: if (a) next_state = S1;  
                else next_state = S0;  
            default: next_state = S0;  
        endcase
```
  
```
    assign y = (state==S3);  
endmodule
```




Mealy Machine Design

1 Assigning binary codes to sates

$S_0 \rightarrow 00$

$S_1 \rightarrow 01$


$S_2 \rightarrow 10$

 

- State coding is not unique and will affect the design

Mealy Machine Design

 - 1 Assigning binary codes to states
- 2 Obtain the binary-coded state table



Mealy Machine Design


- 1 Assigning binary codes to states
- 2 Obtain the binary-coded state table
- 3 Obtain the equations for flip flops inputs and outputs

Present State		Input	Next State		Output
S_1	S_0	x	S'_1	S'_0	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	1
1	0	1	0	1	0
1	1	X	X	X	X

$S'_0 = \overline{S_0}x$
 $S'_1 = S_0x$
 $y = S_1\overline{x}$

Mealy Machine Design

 - 1 Assigning binary codes to states
- 2 Obtain the binary-coded state table
- 3 Obtain the equations for flip flops inputs and outputs
- 4 Draw the logic circuit diagram



SystemVerilog

• Mealy's FSM implementation

```
module mealy_FSM ( input logic clk,  
                  input logic reset,  
                  input logic a,  
                  output logic y );
```



```
    typedef enum logic [1:0] {S0,S1,S2} State;  
    State curr_state, next_state;
```

```
    always_ff @(posedge clk, posedge reset)  
    |      if (reset) curr_state <= S0;  
    |      else curr_state <= next_state;
```


```
    always_comb  
    |      case (curr_state)  
    |      |      S0: if (a) next_state = S1;  
    |      |      |      else next_state = S0;  
    |      |      S1: if (a) next_state = S2;  
    |      |      |      else next_state = S0;  
    |      |      S2: if (a) next_state = S1;  
    |      |      |      else next_state = S0;  
    |      |  
    |      |      default: next_state = S0;  
    |      |  
    |      |      endcase
```

```
    always_comb  
    |      case (curr_state)  
    |      |      S0: y = 1'b0;  
    |      |      S1: y = 1'b0;  
    |      |      S2: y = (a) ? 1'b0 : 1'b1;  
    |      |  
    |      |      default: y = 1'b0;  
    |      |  
    |      |      endcase
```


```
endmodule
```

  


Timing Diagram

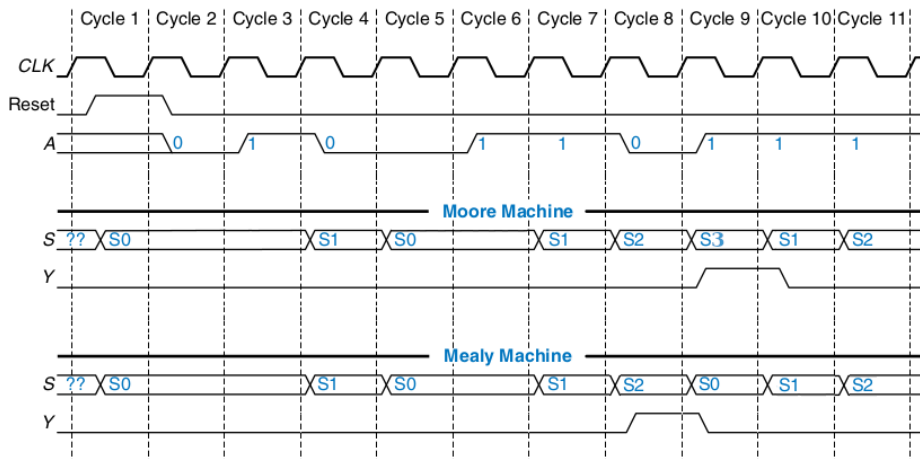

Timing Specification

 


Timing Specification

 


- t_{setup} : It's the time input must have stabilized, before the rising edge

Timing Specification

 


- t_{setup} : It's the time input must have stabilized, before the rising edge
- t_{hold} : It's the time input must have stabilized, after the rising edge

Timing Specification

 


- t_{setup} : It's the time input must have stabilized, before the rising edge
- t_{hold} : It's the time input must have stabilized, after the rising edge
- t_{apv} : It's the sum $t_{setup} + t_{hold}$

Timing Specification

 


- t_{setup} : It's the time input must have stabilized, before the rising edge
- t_{hold} : It's the time input must have stabilized, after the rising edge
- t_{aprr} : It's the sum $t_{setup} + t_{hold}$
- t_{ccq} : It's the contamination delay from the clock to output of the flip flops

Timing Specification

 


- t_{setup} : It's the time input must have stabilized, before the rising edge
- t_{hold} : It's the time input must have stabilized, after the rising edge
- t_{apr} : It's the sum $t_{setup} + t_{hold}$
- t_{ccq} : It's the contamination delay from the clock to output of the flip flops
- t_{pcq} : It's the propagation delay from the clock to output of the flip flops

Timing Specification

 


- t_{setup} : It's the time input must have stabilized, before the rising edge
- t_{hold} : It's the time input must have stabilized, after the rising edge
- t_{aprr} : It's the sum $t_{setup} + t_{hold}$
- t_{ccq} : It's the contamination delay from the clock to output of the flip flops
- t_{pcq} : It's the propagation delay from the clock to output of the flip flops
- The clock cycle T_c must be long enough for all the signals to be settled

Timing Specification

 

- t_{setup} : It's the time input must have stabilized, before the rising edge
- t_{hold} : It's the time input must have stabilized, after the rising edge
- t_{apr} : It's the sum $t_{setup} + t_{hold}$
- t_{ccq} : It's the contamination delay from the clock to output of the flip flops
- t_{pcq} : It's the propagation delay from the clock to output of the flip flops
- The clock cycle T_c must be long enough for all the signals to be settled
- The clock frequency is given by $F_c = \frac{1}{T_c}$


Timing Specification

 

- t_{setup} : It's the time input must have stabilized, before the rising edge
- t_{hold} : It's the time input must have stabilized, after the rising edge
- t_{apr} : It's the sum $t_{setup} + t_{hold}$
- t_{ccq} : It's the contamination delay from the clock to output of the flip flops
- t_{pcq} : It's the propagation delay from the clock to output of the flip flops
- The clock cycle T_c must be long enough for all the signals to be settled
- The clock frequency is given by $F_c = \frac{1}{T_c}$


Timing Specification

 - Determine the minimum clock cycle in the following circuit




Timing Specification

 - Determine the minimum clock cycle in the following circuit




 - Based on the following timing constraints,




Timing Specification

 - Determine the minimum clock cycle in the following circuit



 - Based on the following timing constraints,




We must have:



$$T_c \geq t_{pcq} + t_{pd} + t_{setup}$$

Timing Specification

 - Determine the minimum clock cycle in the following circuit



  - Based on the following timing constraints,




We must have:

$$T_c \geq t_{pcq} + t_{pd} + t_{setup}$$

$$t_{hold} \leq t_{ccq} + t_{cd}$$



Timing Specification (Example)

 - Determine the max and min delay for the given circuit




Timing Specification (Example)

  - Determine the max and min delay equation for the given circuit




Timing Specification (Example)

 - Determine the max and min delay equation for the given circuit



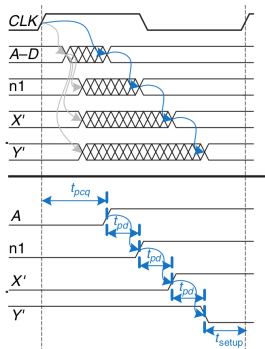
$$T_c \geq t_{pcq} + 3t_{pd} + t_{setup}$$




Timing Specification (Example)

 - Determine the max and min delay equation for the given circuit




$$T_c \geq t_{pcq} + 3t_{pd} + t_{setup}$$

$$t_{hold} \leq t_{ccq} + t_{cd}$$

 

 Question

- Determine the maximum F_c and maximum tolerable t_{hold} for the following circuit



Flip Flop	t_{ccq} (ps)	t_{pcq} (ps)	t_{setup} (ps)	t_{hold} (ps)
	30	80	50	?

Gate	t_{pd} (ps)	t_{cd} (ps)
2-input NAND	20	15
3-input NAND	30	25
2-input NOR	30	25
2-input OR	40	30

$$F_{max} = ?$$

$$t_{hold} = ?$$